

## Electronic Circuits

Prof. Nizamettin AYDIN

[naydin@yildiz.edu.tr](mailto:naydin@yildiz.edu.tr)

<http://www.yildiz.edu.tr/~naydin>

Dr. Gökhan Bilgin

[gokhanb@ce.yildiz.edu.tr](mailto:gokhanb@ce.yildiz.edu.tr)

1

## FET Amplifiers

FETs provide:

- Excellent voltage gain
- High input impedance
- Low-power consumption
- Good frequency range

2

## FET Small-Signal Model

### Transconductance


The relationship of a change in  $I_D$  to the corresponding change in  $V_{GS}$  is called **transconductance**

Transconductance is denoted  $g_m$  and given by:

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

3

## Graphical Determination of $g_m$

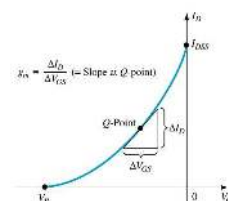

4

## Mathematical Definitions of $g_m$

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

Where  $V_{GS} = 0V$   $g_{m0} = \frac{2I_{DSS}}{|V_P|}$

$$g_m = g_{m0} \left[ 1 - \frac{V_{GS}}{V_P} \right]$$

Where  $1 - \frac{V_{GS}}{V_P} = \sqrt{\frac{I_D}{I_{DSS}}}$

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_P} \right) = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

5

## FET Impedance

Input impedance:

$$Z_i = \infty \Omega$$

Output Impedance:

$$Z_o = r_d = \frac{1}{y_{os}}$$


where:

$$r_d = \frac{\Delta V_{DS}}{\Delta I_D} \Big|_{V_{GS} = \text{constant}}$$

$y_{os}$  = admittance parameter listed on FET specification sheets.

6

## FET AC Equivalent Circuit


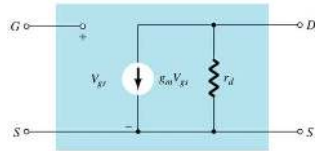


7
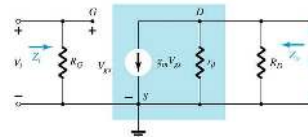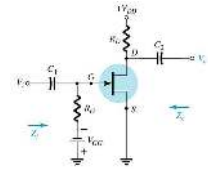
## Common-Source (CS) Fixed-Bias Circuit

The input is on the gate and the output is on the drain

There is a 180° phase shift between input and output



8

## Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:


$$Z_o = R_D \parallel r_d$$

$$Z_o \approx R_D \quad r_d \geq 10R_D$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$
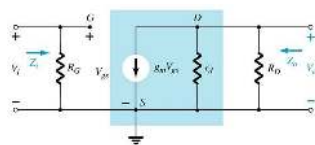
$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad r_d \geq 10R_D$$





9
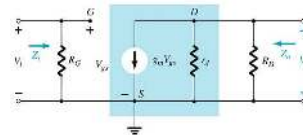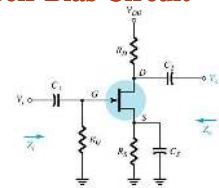
## Common-Source (CS) Self-Bias Circuit

This is a common-source amplifier configuration, so the input is on the gate and the output is on the drain

There is a 180° phase shift between input and output



10

## Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:


$$Z_o = r_d \parallel R_D$$

$$Z_o \approx R_D \quad r_d \geq 10R_D$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$



$$A_v = -g_m R_D \quad r_d \geq 10R_D$$

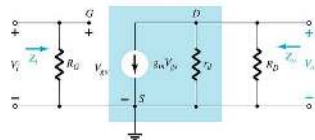

11
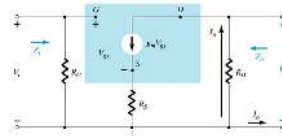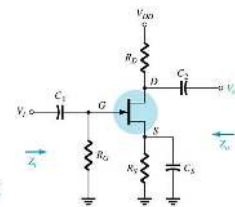
## Common-Source (CS) Self-Bias Circuit

Removing  $C_s$  affects the gain of the circuit.



12

## Calculations

Input impedance:

$$Z_i = R_G$$

Output impedance:

$$Z_o \cong R_D \quad | \quad r_d \geq 10R_D$$

Voltage gain:


$$A_v = \frac{V_o}{V_i} = -\frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

$$A_v = \frac{V_o}{V_i} = -\frac{g_m R_D}{1 + g_m R_S} \quad | \quad r_d \geq 10(R_D + R_S)$$

13
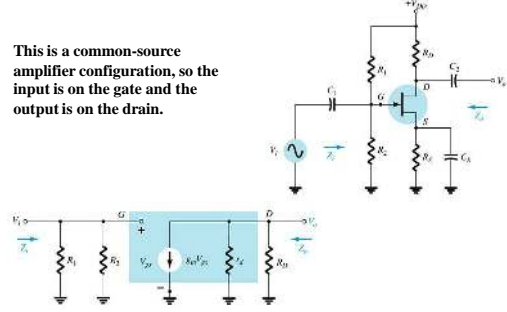
## Common-Source (CS) Voltage-Divider Bias

This is a common-source amplifier configuration, so the input is on the gate and the output is on the drain.



14

## Impedances

Input impedance:

$$Z_i = R_1 \parallel R_2$$

Output impedance:

$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad | \quad r_d \geq 10R_D$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$


$$A_v = -g_m R_D \quad | \quad r_d \geq 10R_D$$

15
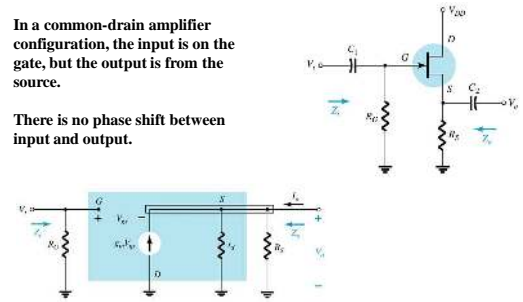
## Source Follower (Common-Drain) Circuit

In a common-drain amplifier configuration, the input is on the gate, but the output is from the source.

There is no phase shift between input and output.



16

## Impedances

Input impedance:

$$Z_i = R_G$$

Output impedance:

$$Z_o = r_d \parallel R_S \parallel \frac{1}{g_m}$$

$$Z_o \cong R_S \parallel \frac{1}{g_m} \quad | \quad r_d \geq 10R_S$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$$


$$A_v = \frac{V_o}{V_i} = \frac{g_m R_S}{1 + g_m R_S} \quad | \quad r_d \geq 10$$

17
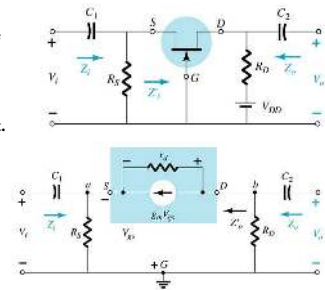
## Common-Gate (CG) Circuit

The input is on the source and the output is on the drain.

There is no phase shift between input and output.



18

## Calculations

**Input impedance:**

$$Z_i = R_S \parallel \left[ \frac{r_d + R_D}{1 + g_m r_d} \right]$$

$$Z_i \approx R_S \parallel \frac{1}{g_m} \quad | r_d \gg 10R_D$$

**Output impedance:**

$$Z_o = R_D \parallel r_d$$


$$Z_o \approx R_D \quad | r_d \gg 10$$

**Voltage gain:**

$$A_v = \frac{V_o}{V_i} = \frac{[g_m R_D + \frac{R_D}{r_d}]}{[1 + \frac{R_D}{r_d}]} \quad A_v \approx g_m R_D \quad | r_d \gg 10R_D$$

19


## D-Type MOSFET AC Equivalent

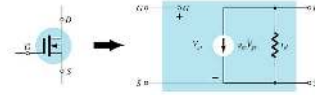

20
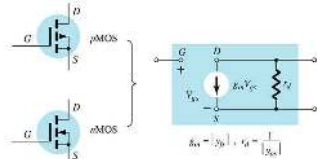
## E-Type MOSFET AC Equivalent


$g_m$  and  $r_d$  can be found in the specification sheet for the FET.



21
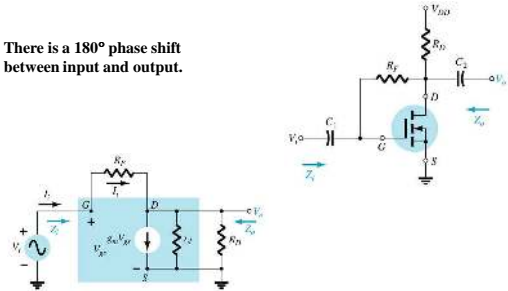
## Common-Source Drain-Feedback

There is a  $180^\circ$  phase shift between input and output.



22

## Calculations

**Input impedance:**

$$Z_i = \frac{R_F + r_d \parallel R_D}{1 + g_m (r_d \parallel R_D)}$$

$$Z_i \approx \frac{R_F}{1 + g_m R_D} \quad | R_F \gg r_d \parallel R_D, r_d \gg 10R_D$$

**Output impedance:**

$$Z_o = R_F \parallel r_d \parallel R_D$$

$$Z_o \approx R_D \quad | R_F \gg r_d \parallel R_D, r_d \gg 10R_D$$


**Voltage gain:**

$$A_v = -g_m (R_F \parallel r_d \parallel R_D)$$

$$A_v \approx -g_m R_D \quad | R_F \gg r_d \parallel R_D, r_d \gg 10R_D$$

23

## Common-Source Voltage-Divider Bias

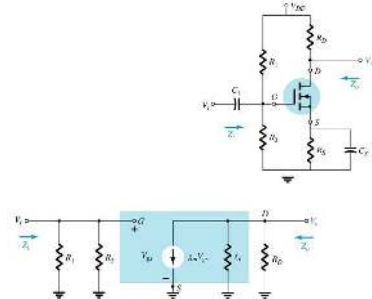

24

## Calculations

**Input impedance:**

$$Z_i = R_1 \parallel R_2$$

**Output impedance:**


$$Z_o = r_d \parallel R_D$$

$$Z_o \approx R_D \mid r_d \geq 10$$

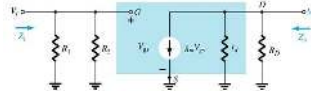**Voltage gain:**

$$A_v = -g_m (r_d \parallel R_D)$$


$$A_v \approx -g_m R_D \mid r_d \geq 10 R_D$$




25

## Summary Table


Source-follower  
[JFET or D-MOSFET]

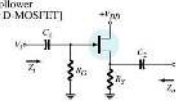


Drain Feedback bias  
E-MOSFET

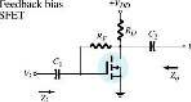

Common-gate  
[JFET or D-MOSFET]

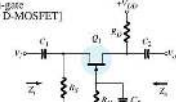

Voltage-divider bias  
E-MOSFET

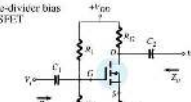


more...


26

## Summary Table


Fixed-bias  
[JFET or D-MOSFET]

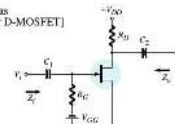

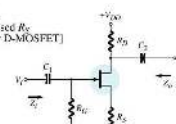
Self-bias  
Unbypassed  $R_S$   
[JFET or D-MOSFET]



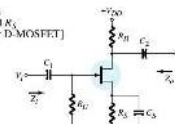Self-bias  
bypassed  $R_S$   
[JFET or D-MOSFET]



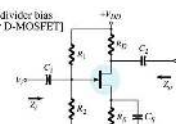Voltage-divider bias  
[JFET or D-MOSFET]



27

## Troubleshooting

**Check the DC bias voltages:**

If not correct check power supply, resistors, FET. Also check to ensure that the coupling capacitor between amplifier stages is OK.

**Check the AC voltages:**

If not correct check FET, capacitors and the loading effect of the next stage

28

## Practical Applications

Three-Channel Audio Mixer

Silent Switching

Phase Shift Networks

Motion Detection System

29