
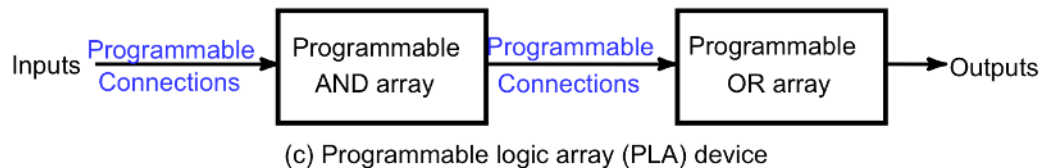
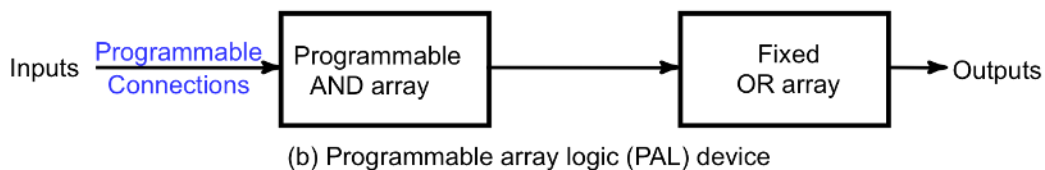


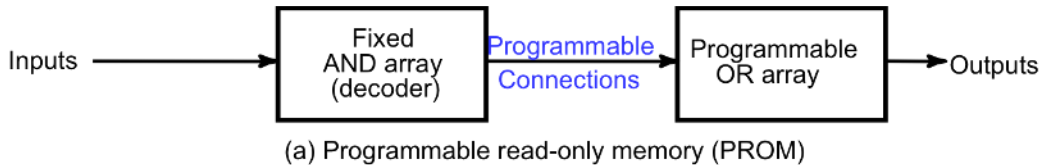
## PROGRAMMABLE LOGIC DEVICES

- **Read Only Memory (ROM)** - a fixed array of AND gates and a programmable array of OR gates
- **Programmable Array Logic (PAL)** - a programmable array of AND gates feeding a fixed array of OR gates.
- **Programmable Logic Array (PLA)** - a programmable array of AND gates feeding a programmable array of OR gates.
- **Complex Programmable Logic Device (CPLD) /Field- Programmable Gate Array (FPGA)** - complex enough to be called “architectures”




### READ ONLY MEMORY

- Read Only Memories (ROM) or Programmable Read Only Memories (PROM) have:
  - N input lines,
  - M output lines, and
  - $2^N$  decoded minterms.
- Fixed AND array with  $2^N$  outputs implementing all N-literal minterms.
- Programmable OR Array with M outputs lines to form up to M sum of minterm expressions.
- A program for a ROM or PROM is simply a multiple-output truth table
  - If a 1 entry, a connection is made to the corresponding minterm for the corresponding output
  - If a 0, no connection is made
- Can be viewed as a *memory* with the inputs as *addresses of data* (output values), hence ROM or PROM names!

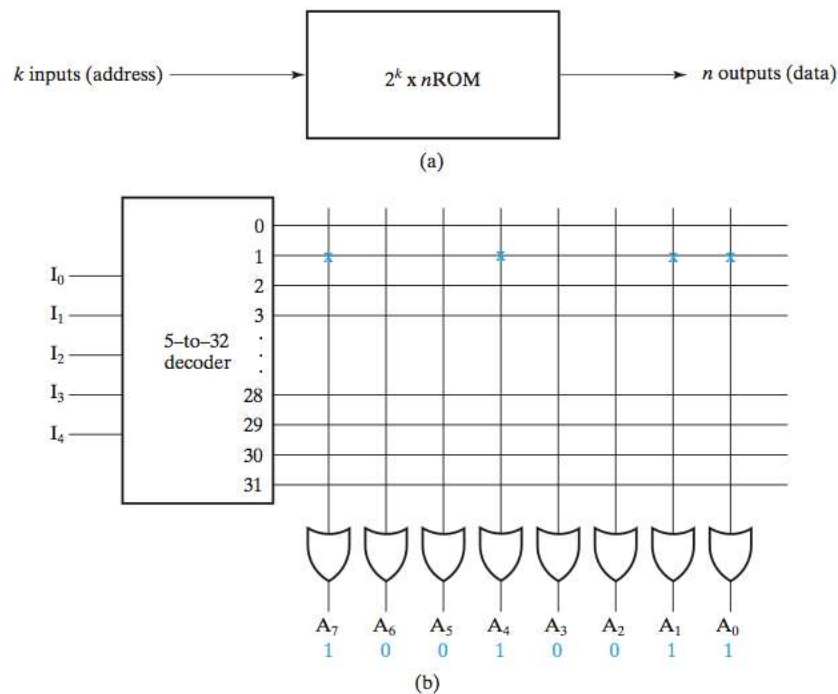

**Figure:** Block diagram and Internal Logic of a ROM

- Depending on the programming technology and approaches, read-only memories have different names
  1. ROM – mask programmed
  2. PROM – fuse or antifuse programmed
  3. EPROM – erasable floating gate programmed
  4. EEPROM or E<sup>2</sup>PROM – electrically erasable floating gate programmed
  5. FLASH memory: electrically erasable floating gate with multiple erasure and programming modes.
- Example: A 8 X 4 ROM (N = 3 input lines, M= 4 output lines)
  - The fixed "AND" array is a "decoder" with 3 inputs and 8 outputs implementing minterms.
  - The programmable "OR" array uses a single line to represent all inputs to an OR gate. An "X" in the array corresponds to attaching the minterm to the OR
  - Read Example: For input (A<sub>2</sub>,A<sub>1</sub>,A<sub>0</sub>) = 001, output is (F<sub>3</sub>,F<sub>2</sub>,F<sub>1</sub>,F<sub>0</sub>) = 0011.
  - What are functions F<sub>3</sub>, F<sub>2</sub>, F<sub>1</sub> and F<sub>0</sub> in terms of (A<sub>2</sub>, A<sub>1</sub>, A<sub>0</sub>)?

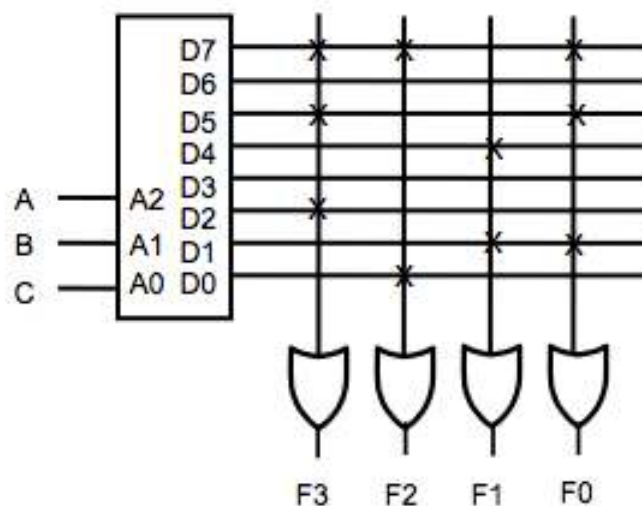


## PROGRAMMABLE LOGIC ARRAY (PLA)

- Compared to a ROM and a PAL, a PLA is the most flexible having a programmable set of ANDs combined with a programmable set of ORs.
- Advantages
  - A PLA can have large N and M permitting implementation of equations that are impractical for a ROM (because of the number of inputs, N, required)
  - A PLA has all of its product terms connectable to all outputs, overcoming the problem of the limited inputs to the PAL Ors
  - Some PLAs have outputs that can be complemented, adding POS functions
- Disadvantages
  - Often, the product term count limits the application of a PLA.
  - Two-level multiple-output optimization is required to reduce the number of product terms in an implementation, helping to fit it into a PLA.
  - Multi-level circuit capability available in PAL not available in PLA. PLA requires external connections to do multi-level circuits.

### Programmable Logic Array Example

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

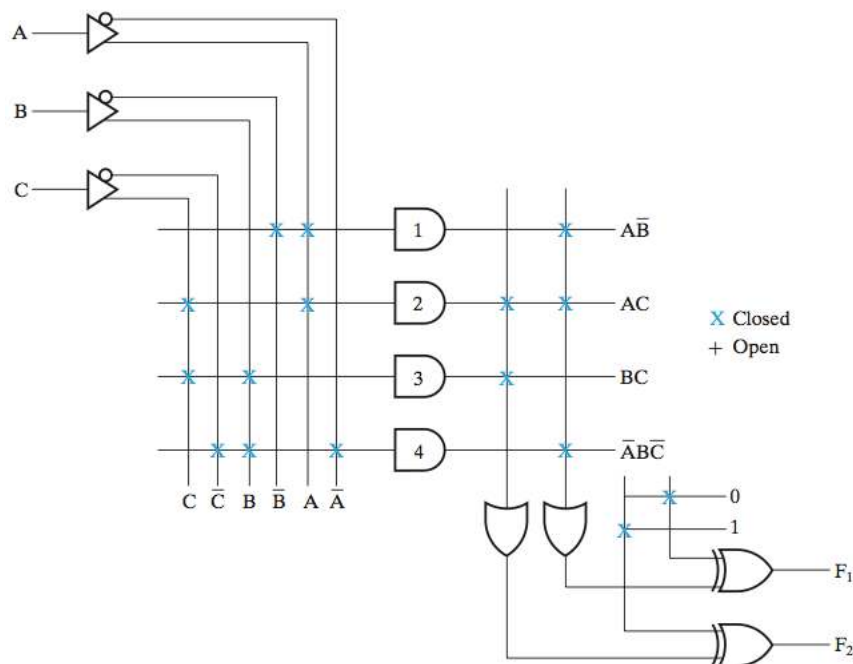


- What are the equations for F<sub>1</sub> and F<sub>2</sub>?
- Could the PLA implement the functions without the XOR gates?
- 3-input, 3-output PLA with 4 product terms

### Example 6-3 from Mano: Implementing a Combinational Circuit Using a PLA

$$F_1(A,B,C) = \Sigma m(3,5,6,7)$$

$$F_2(A,B,C) = \Sigma m(1,2,3,7)$$

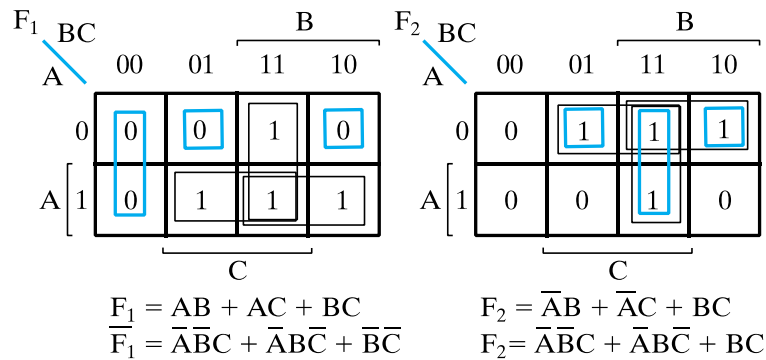

The solution is:

$$F_1 = \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{B}\overline{C}$$

$$F_2 = \overline{A}\overline{B}C + \overline{A}B\overline{C} + BC$$

### PROGRAMMABLE ARRAY LOGIC (PAL)

- The PAL is the opposite of the ROM, having a programmable set of ANDs combined with fixed ORs.
- Disadvantage
  - ROM guaranteed to implement any M functions of N inputs. PAL may have too few inputs to the OR gates.
- Advantages
  - For given internal complexity, a PAL can have larger N and M
  - Some PALs have outputs that can be complemented, adding POS functions
  - No multilevel circuit implementations in ROM (without external connections from output to input). PAL has outputs from OR terms as internal inputs to all AND terms, making implementation of multi-level circuits easier.

#### Programmable Array Logic Example

- 4-input, 3-output PAL with fixed, 3-input OR terms
- What are the equations for F1 through F4?

$$W(A,B,C,D) = \Sigma m(2,12,13)$$

$$X(A,B,C,D) = \Sigma m(7,8,9,10,11,12,13,14,15)$$

$$Y(A,B,C,D) = \Sigma m(0,2,3,4,5,6,7,8,10,11,15)$$

$$Z(A,B,C,D) = \Sigma m(1,2,8,12,13)$$

Simplifying the four function to a minimum number of terms results in the following Boolean functions

$$W = ABC' + A'B'CD'$$

$$X = A + BCD$$

$$Y = A'B + CD + B'D'$$

$$Z = ABC' + A'B'CD' + AC'D' + A'B'C'D = W + AC'D' + A'B'C'D$$

