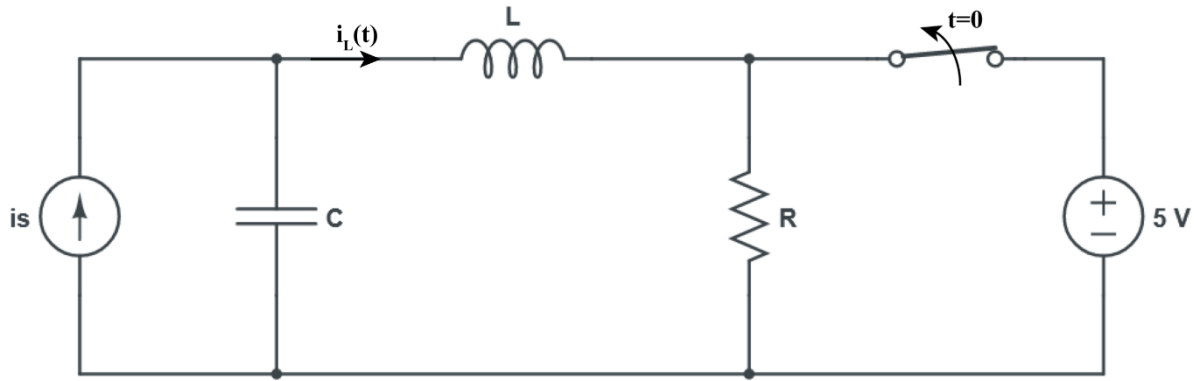


Upload your answer as a single PDF file at max. 5MB of size.

For the given circuit switch is opened at $t=0$ after being closed for a long time.

$R=40\ \Omega$, $C=25\text{mF}$, $L=10\text{H}$



1) If $i_s(t) = 10\ u(t)\text{A}$

a. $i_L(0^-) = ?$


b. $i_L(t) = ?$

2) If $i_s(t) = e^{-3t}\ u(t)\text{A}$

a. $i_L(\infty) = ?$

b. $i_L(t) = ?$

1a) for $t=0^-$ circuit becomes:

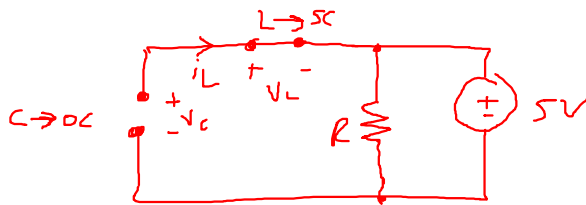

SC: short circuit

OC: open circuit


$$i_L(0^-) = 0\text{A}$$

$$V_C(0^-) = 5\text{V}$$

$$V_L(0^-) = 0\text{V}$$

$$i_C(0^-) = 0\text{A}$$

1b) for $t>0$ circuit becomes

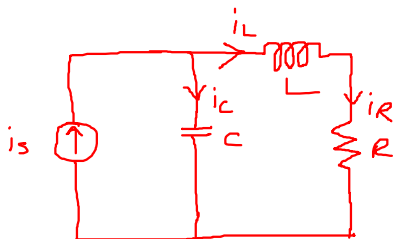

$$i_s = i_L + i_C$$

$$i_R = i_L$$

$$i_C = C \cdot \frac{dV_C}{dt}$$

$$V_L + V_R = V_C$$

$$L \cdot \frac{di_L}{dt} + i_L \cdot R = V_C$$

$$i_c = C \cdot \frac{d}{dt} (L i_L' + R i_L) = CL i_L'' + RC i_L'$$

$$CL i_L'' + RC i_L' + i_L = i_s \quad i_s(t) = 10$$

$$i_L'' + \frac{R}{L} i_L' + \frac{1}{CL} i_L = \frac{i_s}{CL}$$

$$i_L \begin{cases} \rightarrow \text{natural solution} \Rightarrow i_L'' + 4 i_L' + 4 i_L = 0 \Rightarrow i_L = A \cdot e^{\alpha t} \\ \rightarrow \text{forced solution} \Rightarrow i_L = B \end{cases}$$

$$(\alpha^2 + 4\alpha + 4) A \cdot e^{\alpha t} = 0 \Rightarrow \alpha_{1,2} = -2$$

$$i_{L1}(t) = A_1 \cdot e^{-2t}$$

$$i_{L2}(t) = A_2 t \cdot e^{-2t}$$

$$4 \cdot B = 4 \cdot 10 \Rightarrow B = 10$$

$$\Rightarrow i_L(t) = A_1 e^{-2t} + A_2 t e^{-2t} + 10$$

$$\bullet i_L(0^+) = i_L(0) = 0 \text{ A}$$

$$A_1 + 10 = 0 \Rightarrow A_1 = -10$$

$$\bullet v_c(0^-) = 5 \text{ V}$$

$$L \cdot i_L' + R i_L = v_c$$

$$i_L'(0) = \frac{v_c - R i_L(0)}{L} = \frac{5 - 40 \cdot 0}{10} = 0,5$$

$$i_L'(t) = -2A_1 e^{-2t} + A_2 e^{-2t} - 2A_2 t e^{-2t}$$

$$i_L'(0) = -2A_1 + A_2 = 0,5$$

$$A_2 = -19,5$$

$$\Rightarrow i_L(t) = -10 \cdot e^{-2t} - 19,5 \cdot t e^{-2t} + 10$$

$$2a) \quad t \rightarrow \infty \quad i_s(t) = e^{-3t} u(t) \rightarrow 0$$

$$i_L(\infty) = 0$$

$$2b) \quad \text{for } t=0 \quad i_L(0)=0 \quad V_L(0)=0 \quad i_C(0)=0 \quad V_C(0)=5$$

$$\text{for } t > 0$$

$$CL i_L'' + R i_L' + i_L = i_s \quad i_s(t) = e^{-3t}$$

$$i_L'' + \frac{R}{L} i_L' + \frac{1}{CL} i_L = \frac{i_s}{CL}$$

$$i_L \begin{cases} \rightarrow \text{natural solution} \Rightarrow i_L'' + 4 i_L' + 4 i_L = 0 \Rightarrow i_{L_n} = A \cdot e^{\alpha t} \\ \rightarrow \text{forced solution} \Rightarrow i_{L_f} = B \cdot e^{-3t} \end{cases}$$

$$i_{L_n}(t) = A_1 \cdot e^{-2t} + A_2 \cdot t \cdot e^{-2t}$$

$$9B e^{-3t} - 12B e^{-3t} + 4B e^{-3t} = 4 \cdot e^{-3t}$$

$$B = 4$$

$$i_{L_f}(t) = 4 e^{-3t}$$

$$i_L(t) = A_1 e^{-2t} + A_2 \cdot t e^{-2t} + 4 \cdot e^{-3t}$$

$$\bullet \quad i_L(0) = 0 \Rightarrow A_1 + 4 = 0 \Rightarrow A_1 = -4$$

$$\bullet \quad i_L'(0) = 0,5$$

$$i_L'(t) = -2A_1 e^{-2t} + A_2 e^{-2t} - 2A_2 t e^{-2t} - 12 e^{-3t}$$

$$i_L'(0) = -2A_1 + A_2 - 12 = 0,5$$

$$-2A_1 + A_2 = 12,5$$

$$A_2 = 4,5$$

$$\Rightarrow i_L(t) = -4 e^{-2t} + 4,5 \cdot t e^{-2t} + 4 e^{-3t}$$