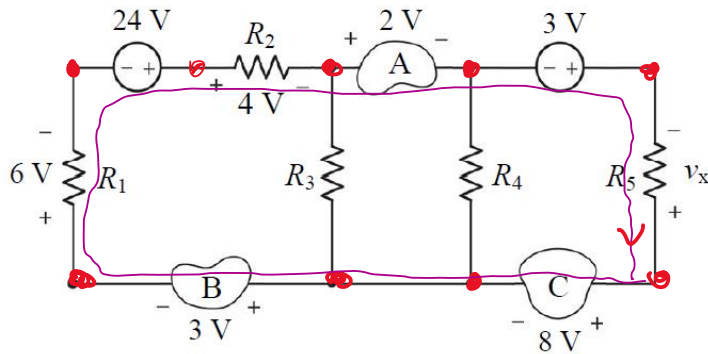


BLM1032 – Circuit Theory
Short Exam 1 – 08/April/2021

Upload your answer as a single PDF file at max. 5MB of size. There are total of 5 (five questions).

Q 1: Parts (a)–(d) refer to the circuit given below.




(a) How many nodes exist in this circuit?

There are total of 8 nodes.

(b) Determine the voltage v_x . (3)

*walking through the given loop: $3 + 3 + 6 - 24 + 4 + 2 - 3 - v_x = 0$
 $v_x = -4V$*

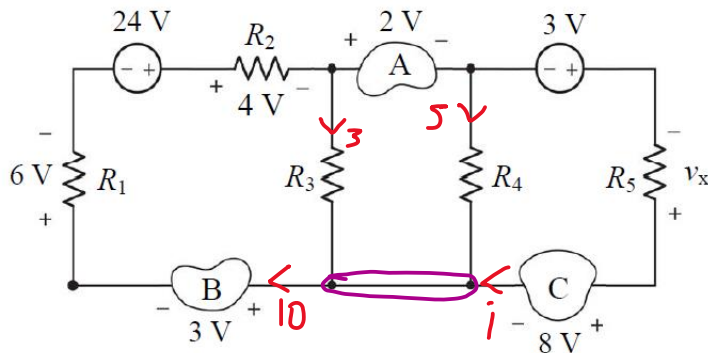(c) If a current of 10 A flows through element B to the left, 3 A flows through R_3 downward, and 5 A flows through R_4 downward, how much current flows through resistor R_5 ? (3)



Writing KCL for the node

$$3 + 5 + i = 10$$

$$i = 2A$$

(d) How much electrical energy is absorbed by resistor R_5 in 7 seconds? (2)

$$E = t \cdot v \cdot i = 7 \cdot 2 \cdot (-4) = 56 \text{ Joules}$$

Q 2: If $R_{eq} = 50 \Omega$ in the circuit in below Figure, find R . (6)


$$R_{eq} = ((12 // 12 // 12) + R + 10) // 60 + 30$$

$$50 = ((4 + R + 10) // 60) + 30$$

$$20 = (14 + R) // 60$$

$$\frac{1}{20} = \frac{1}{14 + R} + \frac{1}{60}$$

$$14 + R = 30 \implies R = 16$$

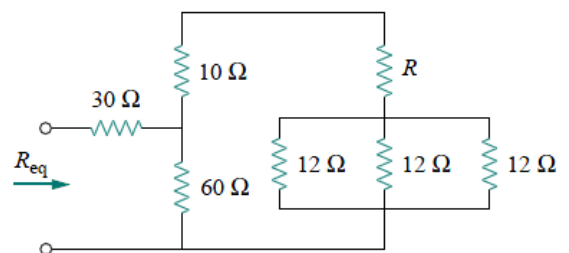


BLM1032 – Circuit Theory
Short Exam 1 – 08/April/2021

Q 3: For the circuit below, the voltage source delivers 50 W. If the value of the current i_x is 9 A, determine the value of the resistance R_x . (8)

$$P \cdot 10 = -50 \Rightarrow I = -5A$$

$$I + i_x + I_y = 7 \Rightarrow -5 + 9 + I_y = 7 \Rightarrow I_y = 3A$$


$$V = 3 \cdot 12k \quad R_x = \frac{V}{i_x} = \frac{3 \cdot 12k}{9} = 4k\Omega$$

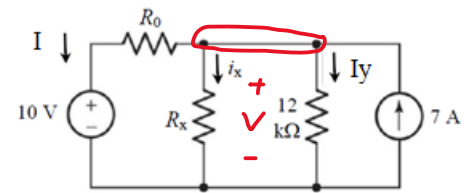

BLM1032 – Circuit Theory

Short Exam 1 – 08/April/2021

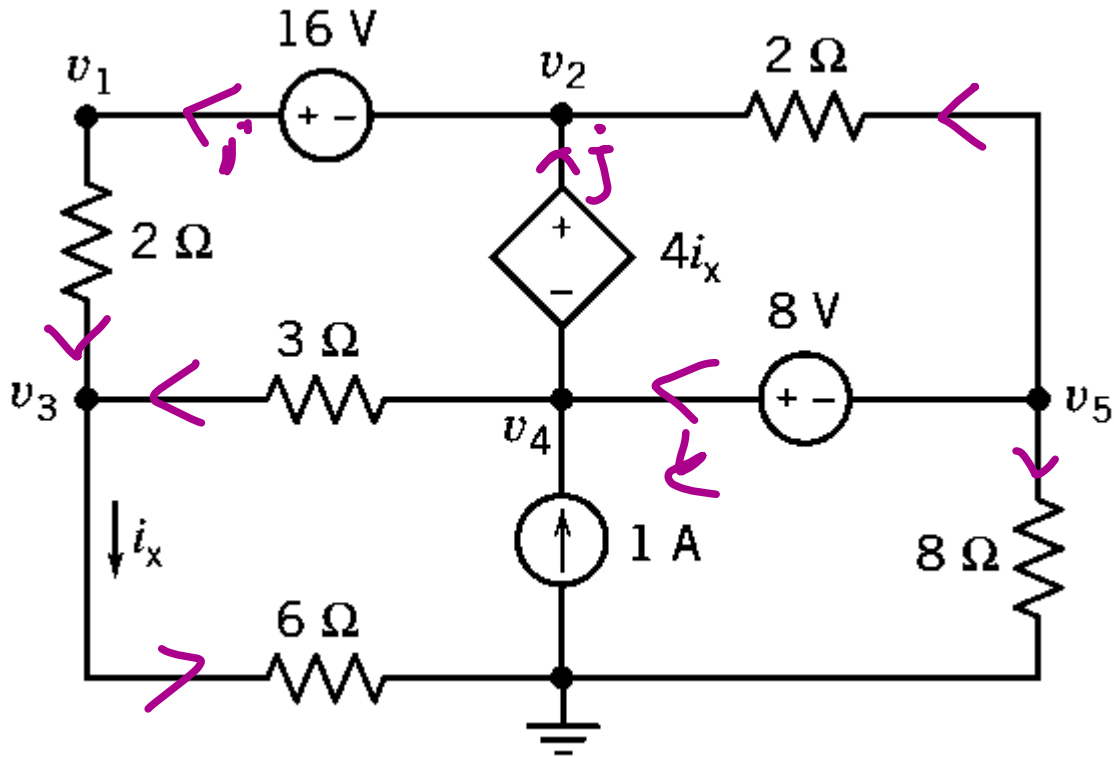Q 4: Write down the equation system for the given circuit using the node analysis method.



$$v_1: \frac{v_1 - v_3}{2} = i$$

$$v_2: \frac{v_5 - v_2}{2} + j - i = 0$$

$$v_3: \frac{v_4 - v_3}{3} + \frac{v_1 - v_3}{2} - \frac{v_3}{6} = 0$$

$$v_4: 1 + k - j - \frac{v_4 - v_3}{3} = 0$$

$$v_5: \frac{v_5}{8} + k + \frac{v_5 - v_2}{2} = 0$$

$$i_x = \frac{v_3}{6}$$

$$v_4 = v_5 + 8$$

$$v_1 = v_2 + 16 \quad v_2 = v_4 + 4i_x$$

$$v_1, v_2, v_3, v_4, v_5, i, j, k, i_x$$

for puan
iam yeteri!

BLM1032 – Circuit Theory
Short Exam 1 – 08/April/2021

$$\begin{array}{lclcl}
 \textcircled{1} & V_1 & -V_3 & -2i & = 0 \\
 \textcircled{2} & -V_2 & +V_5 & -2i + 2j & = 0 \\
 \textcircled{3} & 3V_1 & -6V_3 + 2V_6 & & = 0 \\
 \textcircled{4} & & V_3 - V_6 & -3j + 3k & = -3 \\
 \textcircled{5} & -4V_2 & +5V_4 & +8k & = 0 \\
 \textcircled{6} & & V_3 & -6ix & = 0 \\
 \textcircled{7} & & V_6 - V_5 & & = 8 \\
 \textcircled{8} & & & & = 16 \\
 \textcircled{9} & & V_2 & +4ix & = 0 \\
 & & -V_2 + V_4 & &
 \end{array}$$


$$\begin{bmatrix}
 1 & 0 & -1 & 0 & 0 & -2 & 0 & 0 & 0 \\
 0 & -1 & 0 & 0 & 1 & -2 & 2 & 0 & 0 \\
 3 & 0 & -6 & 2 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & -1 & 0 & 0 & -3 & 3 & 0 \\
 0 & -4 & 0 & 0 & 5 & 0 & 0 & 8 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & -6 \\
 0 & 0 & 0 & 1 & -1 & 0 & 0 & 0 & 0 \\
 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & -1 & 0 & 1 & 0 & 0 & 0 & 0 & 4
 \end{bmatrix}^{-1} \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 -3 \\
 0 \\
 0 \\
 8 \\
 16 \\
 0
 \end{bmatrix} \Rightarrow$$

$$\begin{aligned}
 V_1 &= 24V \\
 V_2 &= 8V \\
 V_3 &= 12V \\
 V_4 &= 0V \\
 V_5 &= -8V \\
 i &= 6A \\
 j &= 16A \\
 k &= 9A \\
 ix &= 2A
 \end{aligned}$$

BLM1032 – Circuit Theory

Short Exam 1 – 08/April/2021

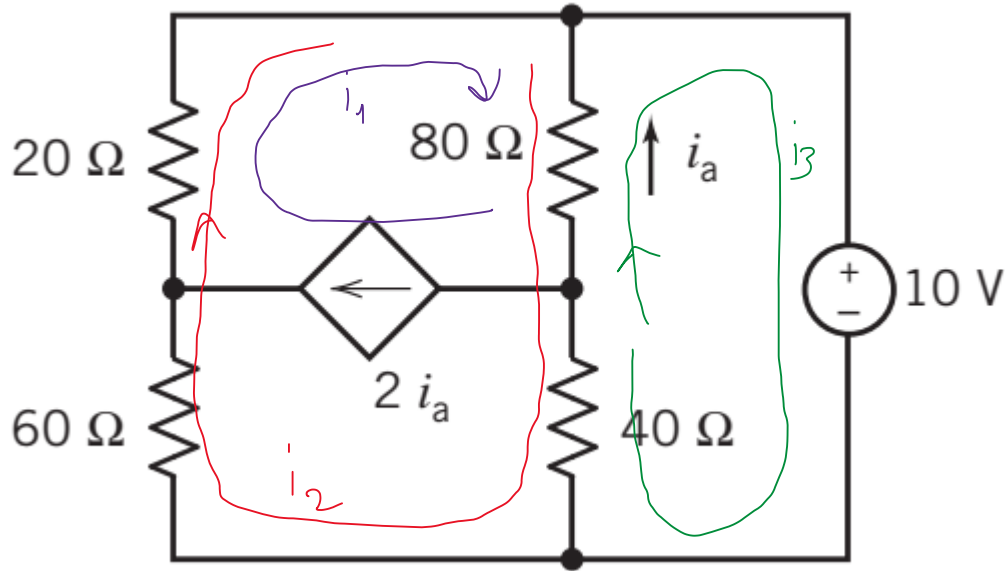Q 5: Write down the equation system for the given circuit using the mesh analysis method.



①

$$i_1 = 2i_a$$

②

$$60i_2 + 20(i_1 + i_2) + 80(i_1 + i_2 - i_3) + 60(i_2 - i_3) = 0$$

③

$$40(i_3 - i_2) + 80(i_3 - i_2 - i_1) + 10 = 0$$

④

$$i_a = i_3 - i_2 - i_1$$

tan puan
tan yeteri

$$\begin{bmatrix} 1 & 0 & 0 & -2 \\ 100 & 100 & -180 & 0 \\ -80 & -120 & 120 & 0 \\ 1 & 1 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_a \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -10 \\ 0 \end{bmatrix}$$

$$i_1 = -0,1 A$$

$$i_2 = -0,1 A$$

$$i_3 = -0,25 A$$

$$i_a = -0,05 A$$