

## Electronic Circuits

Prof. Nizamettin AYDIN

[naydin@yildiz.edu.tr](mailto:naydin@yildiz.edu.tr)

<http://www.yildiz.edu.tr/~naydin>

Dr. Gökhan Bilgin

[gokhanb@ce.yildiz.edu.tr](mailto:gokhanb@ce.yildiz.edu.tr)

1

## Common FET Biasing Circuits

### JFET Biasing Circuits

- Fixed – Bias
- Self-Bias
- Voltage-Divider Bias

### D-Type MOSFET Biasing Circuits

- Self-Bias
- Voltage-Divider Bias

### E-Type MOSFET Biasing Circuits

- Feedback Configuration
- Voltage-Divider Bias

2

## Basic Current Relationships

For all FETs:

$$I_G \cong 0A$$

$$I_D = I_S$$

For JFETs and D-Type MOSFETs:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

For E-Type MOSFETs:

$$I_D = k(V_{GS} - V_T)^2$$

3

## Fixed-Bias Configuration


$$V_{DS} = V_{DD} - I_D R_D$$

$$V_S = 0V$$

$$V_C = V_{DS}$$


$$V = V_{GS}$$

$$V_{GS} = -V_{GG}$$

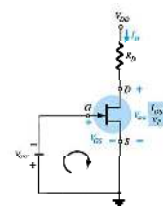

4

## Self-Bias Configuration

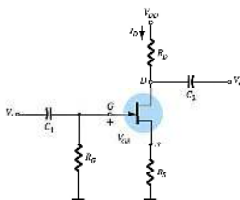

5

## Self-Bias Calculations

For the indicated loop,  $V_{GS} = -I_D R_S$

To solve this equation:


- Select an  $I_D < I_{DSS}$  and use the component value of  $R_S$  to calculate  $V_{GS}$ .
- Plot the point identified by  $I_D$  and  $V_{GS}$ . Draw a line from the origin of the axis to this point.
- Plot the transfer curve using  $I_{DSS}$  and  $V_P$  ( $V_P = V_{GSoff}$  in specification sheets) points such as  $I_D = I_{DSS}/4$  and  $I_D = I_{DS}$ .

The Q-point is located where the first line intersects the transfer curve. Use the value of  $I_D$  at the Q-point ( $I_{DQ}$ ) to solve for the other voltages:

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_D = V_{DS} + V_S = V_{DD} - V_{RD}$$

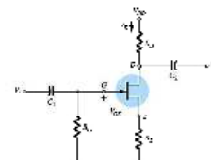


6
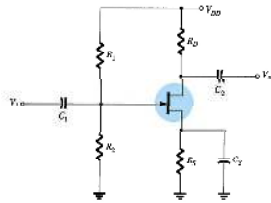
## Voltage-Divider Bias

$I_G = 0$  A

$I_D$  responds to changes in  $V_{GS}$ .



7

## Voltage-Divider Bias Calculations


$V_G$  is equal to the voltage across divider resistor  $R_2$ :

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

Using Kirchhoff's Law:

$$V_{GS} = V_G - I_D R_S$$

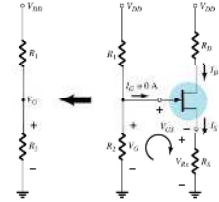The Q point is established by plotting a line that intersects the transfer curve.



8

## Voltage-Divider Q-point

### Step 1

Plot the line by plotting two points:


- $V_{GS} = V_G$ ,  $I_D = 0$  A
- $V_{GS} = 0$  V,  $I_D = V_G / R_S$

### Step 2

Plot the transfer curve by plotting  $I_{DSS}$ ,  $V_P$  and the calculated values of  $I_D$
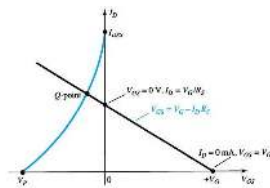
### Step 3

The Q-point is located where the line intersects the transfer curve



9

## Voltage-Divider Bias Calculations

Using the value of  $I_D$  at the Q-point, solve for the other variables in the voltage-divider bias circuit:

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$


$$V_S = I_D R_S$$

$$I_{R1} = I_{R2} = \frac{V_{DD}}{R_1 + R_2}$$

10
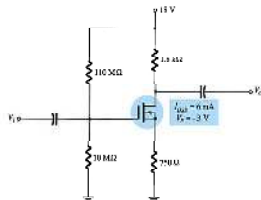
## D-Type MOSFET Bias Circuits

Depletion-type MOSFET bias circuits are similar to those used to bias JFETs. The only difference is that depletion-type MOSFETs can operate with positive values of  $V_{GS}$  and with  $I_D$  values that exceed  $I_{DSS}$ .



11

## Self-Bias

### Step 1

Plot line for

- $V_{GS} = V_G$ ,  $I_D = 0$  A
- $I_D = V_G / R_S$ ,  $V_{GS} = 0$  V


### Step 2

Plot the transfer curve using  $I_{DSS}$ ,  $V_P$  and calculated values of  $I_D$
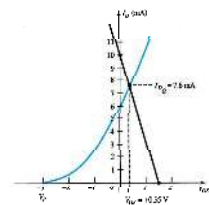
### Step 3

The Q-point is located where the line intersects the transfer curve. Use the  $I_D$  at the Q-point to solve for the other variables in the voltage-divider bias circuit.

These are the same steps used to analyze JFET self-bias circuits.



12

## Voltage-Divider Bias

### Step 1

Plot the line for

- $V_{GS} = V_G$ ,  $I_D = 0$  A
- $I_D = V_G / R_S$ ,  $V_{GS} = 0$  V


### Step 2

Plot the transfer curve using  $I_{DSS}$ ,  $V_P$ , and calculated values of  $I_D$ .
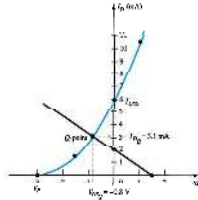
### Step 3

The Q-point is located where the line intersects the transfer curve is. Use the  $I_D$  at the Q-point to solve for the other variables in the voltage-divider bias circuit.


These are the same steps used to analyze JFET voltage-divider bias circuits.



13
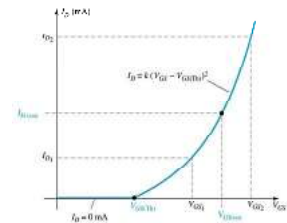
## E-Type MOSFET Bias Circuits

The transfer characteristic for the e-type MOSFET is very different from that of a simple JFET or the d-type MOSFET.



14


## Feedback Bias Circuit

$$I_G = 0 \text{ A}$$

$$V_{RG} = 0 \text{ V}$$

$$V_{DS} = V_{GS}$$

$$V_{GS} = V_{DD} - I_D R_D$$

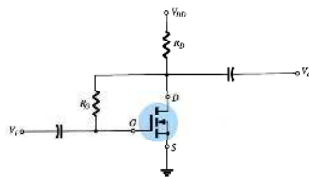

15

## Feedback Bias Q-Point

### Step 1

Plot the line using

- $V_{GS} = V_{DD}$ ,  $I_D = 0$  A
- $I_D = V_{DD} / R_D$ ,  $V_{GS} = 0$  V

### Step 2

Using values from the specification sheet, plot the transfer curve with


- $V_{GSTh} = I_D = 0$  A
- $V_{GS(on)} = I_{D(on)}$

### Step 3

The Q-point is located where the line and the transfer curve intersect
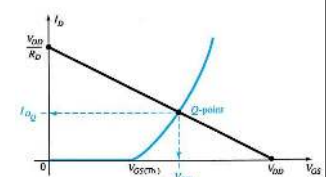
### Step 4

Using the value of  $I_D$  at the Q-point, solve for the other variables in the bias circuit



16


## Voltage-Divider Biasing

Plot the line and the transfer curve to find the Q-point. Use these equations:

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

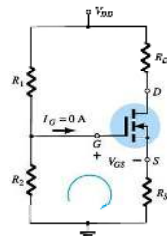

17

## Voltage-Divider Bias Q-Point

### Step 1

Plot the line using

- $V_{GS} = V_G = (R_2 V_{DD}) / (R_1 + R_2)$ ,  $I_D = 0$  A
- $I_D = V_G / R_S$ ,  $V_{GS} = 0$  V

### Step 2

Using values from the specification sheet, plot the transfer curve with

- $V_{GSTh} = I_D = 0$  A
- $V_{GS(on)} = I_{D(on)}$

### Step 3

The point where the line and the transfer curve intersect is the Q-point.

### Step 4

Using the value of  $I_D$  at the Q-point, solve for the other circuit values.

18

## ***p*-Channel FETs**

For *p*-channel FETs the same calculations and graphs are used, except that the voltage polarities and current directions are reversed.

The graphs are mirror images of the *n*-channel graphs.

19

## **Applications**

Voltage-controlled resistor  
JFET voltmeter  
Timer network  
Fiber optic circuitry  
MOSFET relay driver

20