

## Electronic Circuits

Prof. Nizamettin AYDIN

[naydin@yildiz.edu.tr](mailto:naydin@yildiz.edu.tr)

<http://www.yildiz.edu.tr/~naydin>

Dr. Gökhan Bilgin

[gokhanb@ce.yildiz.edu.tr](mailto:gokhanb@ce.yildiz.edu.tr)

1


## Transistor Construction

There are two types of transistors:

- *pnp*
- *npn*

The terminals are labeled:

- E - Emitter
- B - Base
- C - Collector

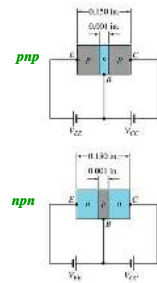


2
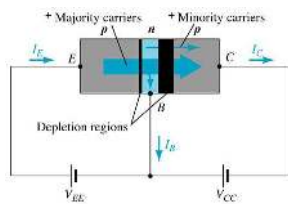
## Transistor Operation

With the external sources,  $V_{EE}$  and  $V_{CC}$ , connected as shown:

- The emitter-base junction is forward biased
- The base-collector junction is reverse biased



3


## Currents in a Transistor

Emitter current is the sum of the collector and base currents:

$$I_E = I_C + I_B$$


The collector current is comprised of two currents:
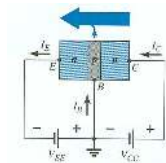
$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$



4

## Common-Base Configuration

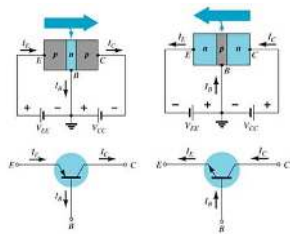


The base is common to both input (emitter-base) and output (collector-base) of the transistor.

5

## Common-Base Amplifier
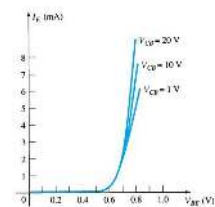
### Input Characteristics

This curve shows the relationship between input current ( $I_E$ ) to input voltage ( $V_{BE}$ ) for three output voltage ( $V_{CB}$ ) levels.




6

## Common-Base Amplifier
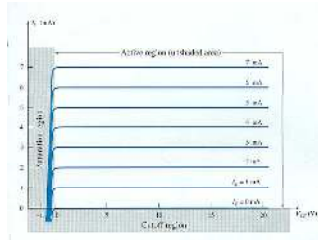
### Output Characteristics

This graph demonstrates the output current ( $I_C$ ) to an output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).



7

## Operating Regions

- **Active** – Operating range of the amplifier.
- **Cutoff** – The amplifier is basically off. There is voltage, but little current.
- **Saturation** – The amplifier is full on. There is current, but little voltage.

8

## Approximations

Emitter and collector currents:

$$I_C \approx I_E$$

Base-emitter voltage:

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$

9

## Alpha ( $\alpha$ )

Alpha ( $\alpha$ ) is the ratio of  $I_C$  to  $I_E$  :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

Ideally:  $\alpha = 1$


In reality:  $\alpha$  is between 0.9 and 0.998

Alpha ( $\alpha$ ) in the AC mode:

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$$

10

## Transistor Amplification

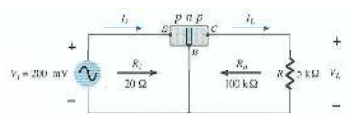

Currents and Voltages:

$$I_E = I_i = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

$$I_C \approx I_E$$

$$I_L \approx I_i = 10 \text{ mA}$$

$$V_L = I_L R = (10 \text{ mA})(5 \text{ k}\Omega) = 50 \text{ V}$$

Voltage Gain:


$$A_v = \frac{V_L}{V_i} = \frac{50 \text{ V}}{200 \text{ mV}} = 250$$

11
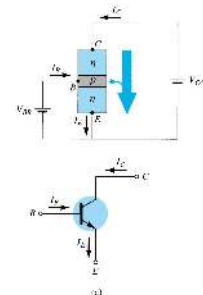
## Common-Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector-emitter).

The input is on the base and the output is on the collector.



12

## Common-Emitter Characteristics

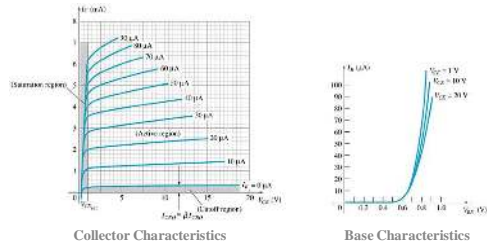

13

## Common-Emitter Amplifier Currents

### Ideal Currents

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

### Actual Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

$I_{CBO}$  is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When  $I_B = 0 \mu A$  the transistor is in cutoff, but there is some minority current flowing called  $I_{CEO}$ .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \quad I_B = 0 \mu A$$

14

## Beta ( $\beta$ )

$\beta$  represents the amplification factor of a transistor. ( $\beta$  is sometimes referred to as  $h_{fe}$ , a term used in transistor modeling calculations)

In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

In AC mode:

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \bigg|_{V_{CE} = \text{constant}}$$


15

## Beta ( $\beta$ )

Determining  $\beta$  from a Graph

$$\begin{aligned} \beta_{AC} &= \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \mu A - 20 \mu A)} \\ &= \frac{1 \text{ mA}}{10 \mu A} \bigg|_{V_{CE} = 7.5} \\ &= 100 \end{aligned}$$

$$\begin{aligned} \beta_{DC} &= \frac{2.7 \text{ mA}}{25 \mu A} \bigg|_{V_{CE} = 7.5} \\ &= 108 \end{aligned}$$

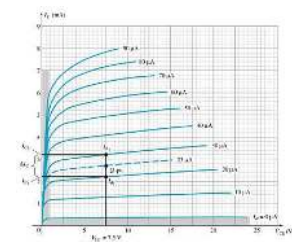

16

## Beta ( $\beta$ )

Relationship between amplification factors  $\beta$  and  $\alpha$

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{\alpha - 1}$$


Relationship Between Currents

$$I_C = \beta I_B \quad I_E = (\beta + 1) I_B$$

17
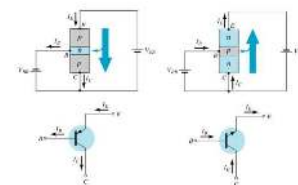
## Common-Collector Configuration


The input is on the base and the output is on the emitter.



18
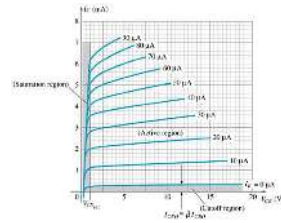
## Common–Collector Configuration

The characteristics are similar to those of the common-emitter configuration, except the vertical axis is  $I_E$ .




19

### Operating Limits for Each Configuration

$V_{CE}$  is at maximum and  $I_C$  is at minimum ( $I_{C_{max}} = I_{CEO}$ ) in the cutoff region.

$I_C$  is at maximum and  $V_{CE}$  is at minimum ( $V_{CE\max} = V_{CEsat} = V_{CE0}$ ) in the saturation region.

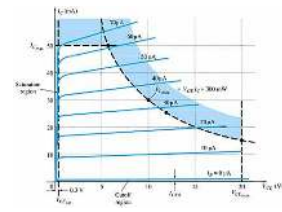The transistor operates in the active region between saturation and cutoff.



20

## Power Dissipation

**Common-base:**

$$P_{Cmax} = V_{CB}I_C$$

**Common-emitter:**

$$P_{Cmax} = V_{CE}I_C$$

**Common-collector:**

$$P_{Cmax} = V_{CE} I_E$$

21

## Transistor Specification Sheet

MAXIMUM RATINGS			
Rating	Symbol	204(2)	Unit
Cathode Power Dissipation	$P_{DCH}$	30	W
Cathode Reverse Voltage	$V_{RCH}$	40	V
Anode-Base Voltage	$V_{AB}$	3.0	V
Cathode Current - Continuous	$I_{CH}$	210	mA
Total Device Dissipation $T_A = 25^\circ\text{C}$	$P_D$	625	mW
Device above $25^\circ\text{C}$		3.0	mW/°C
Operating and Storage Junction Temperature Range	$T_J, T_{STG}$	-55 to +150	°C

THERMAL CHARACTERISTICS			
Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JA}$	0.5	°C/W
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	°C



22


## Transistor Specification Sheet

[illegible]

23
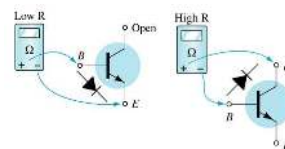
## Transistor Testing

- **Curve Tracer**  
Provides a graph of the characteristic curves.
- **DMM**  
Some DMMs measure  $\beta_{DC}$  or  $h_{FE}$ .
- **Ohmmeter**



24

## Transistor Terminal Identification

# Transistor Terminal Identification