## **BLM2041 Signals and Systems**

### **Syllabus**


The Instructors:

Doç. Dr. Ali Can Karaca ackaraca@yildiz.edu.tr

Dr. Ahmet Elbir aelbiraelbir aelbir a
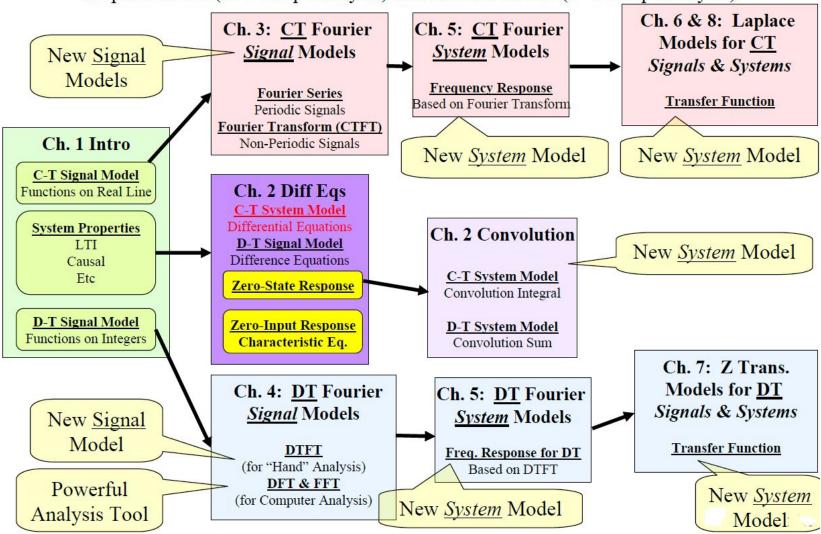
## **Course Flow Diagram**


The arrows here show conceptual flow between ideas. Note the parallel structure between the pink blocks (C-T Freq. Analysis) and the blue blocks (D-T Freq. Analysis).



## System Modeling

To do engineering design, we must be able to accurately predict the quantitative behavior of a circuit or other system.

This requires math models:

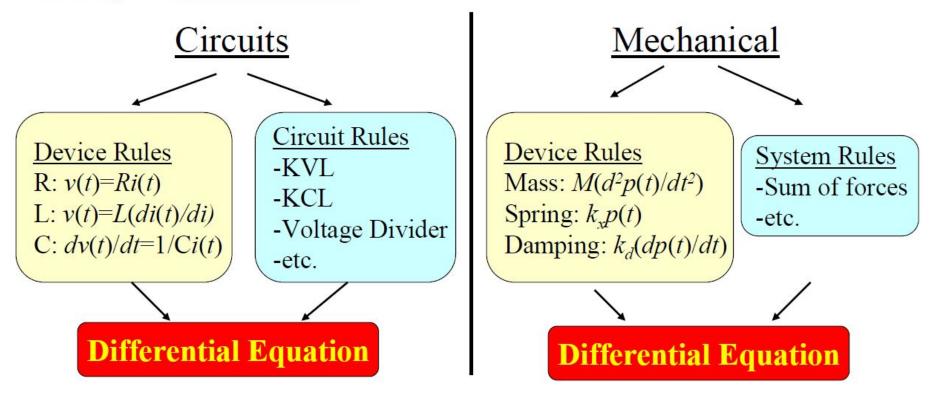


Similar ideas hold for <u>hydraulic</u>, <u>chemical</u>, etc. systems...




"differential equations rule the world"
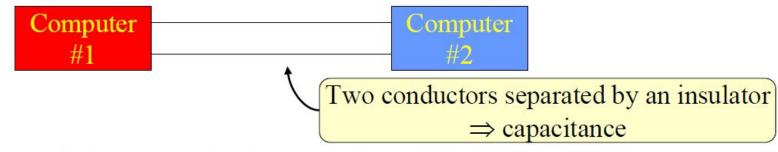
## Simple Circuit Example


Sending info over a wire cable between two computers




### Two practical examples of the cable

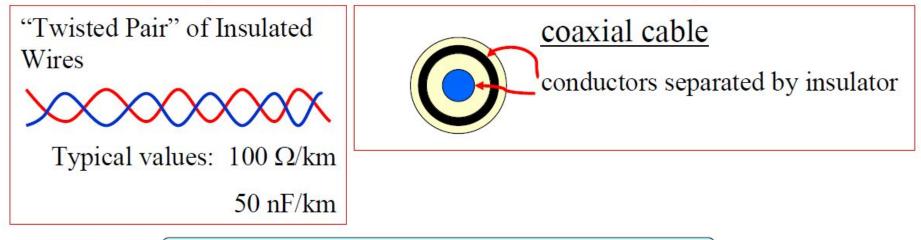


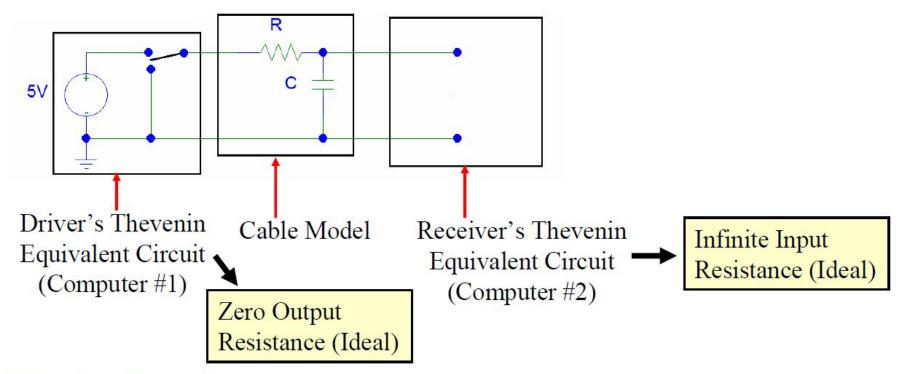Recall: resistance increases with wire length



### **Effective Operation:**

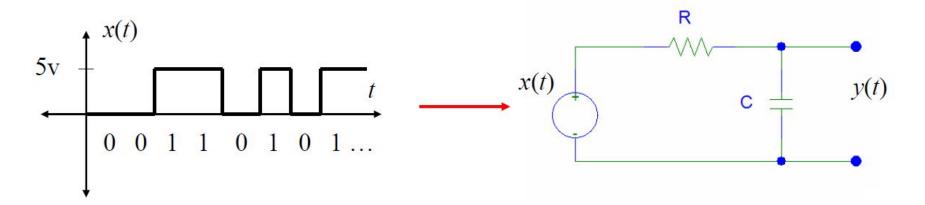

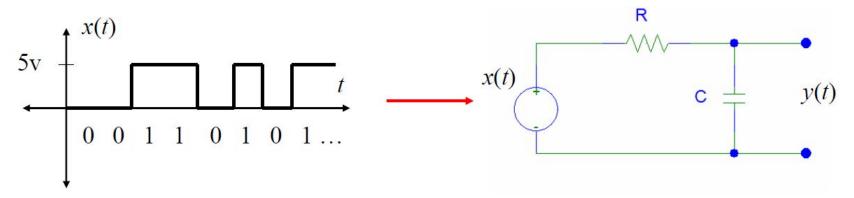

#### **Use Loop Equation & Device Rules:**

$$x(t) = v_R(t) + y(t)$$

$$v_R(t) = Ri(t)$$

$$i(t) = C \frac{dy(t)}{dt}$$




$$\frac{dy(t)}{dt} + \frac{1}{RC}y(t) = \frac{1}{RC}x(t)$$

This is the Differential Equation to be "Solved":

Given: Input x(t)

Find: Solution y(t)

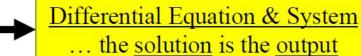
Recall: A "Solution" of the D.E. means... The function that when put into the left side causes it to reduce to the right side





Now... because this is a <u>linear</u> system (it only has R, L, C components!) we

can analyze it by superposition.


Decompose the input...

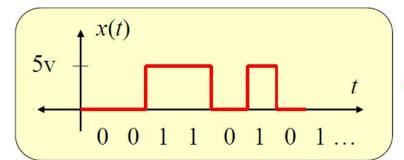

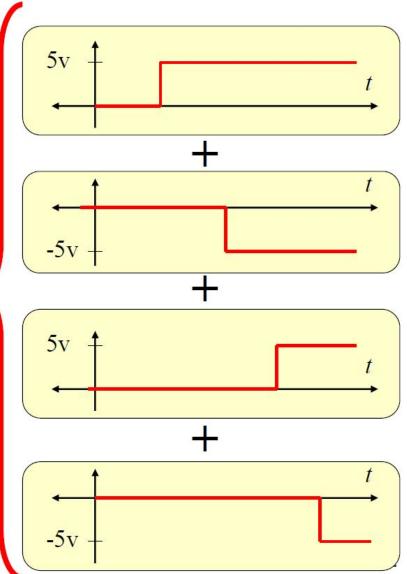


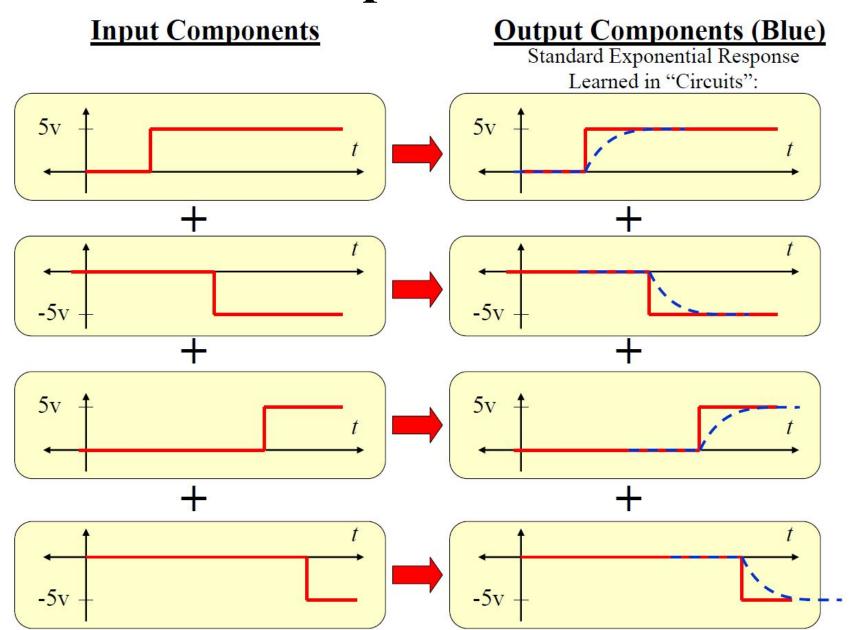

### **Output Components**

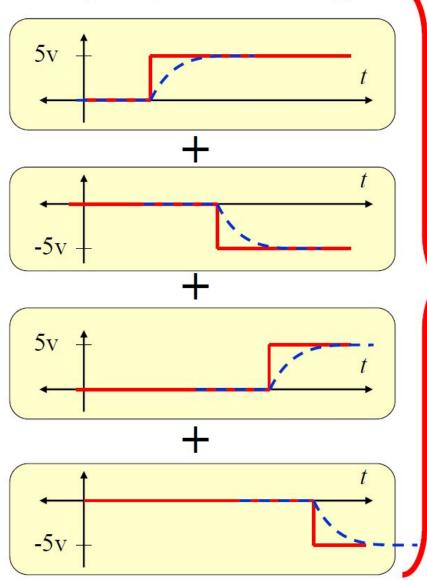

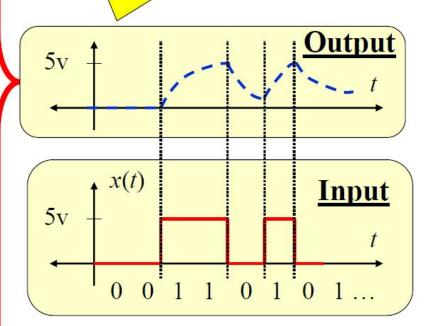Output is a "smoothed" version of the input... it is harder to distinguish "ones" and "zeros"... it will be even harder if there is noise added onto the signal!



# Progression of Ideas an Engineer Might Use for this Problem

### **Physical System:**



### **Schematic System:**




### **Mathematical System:**




### **Mathematical Solution**:




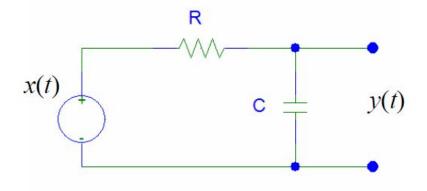
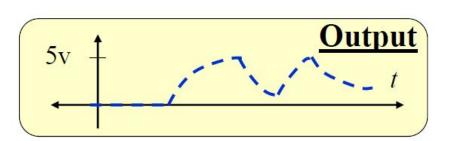
$$\frac{dy(t)}{dt} + \frac{1}{RC}y(t) = \frac{1}{RC}x(t)$$



### Automobile Suspension System Example

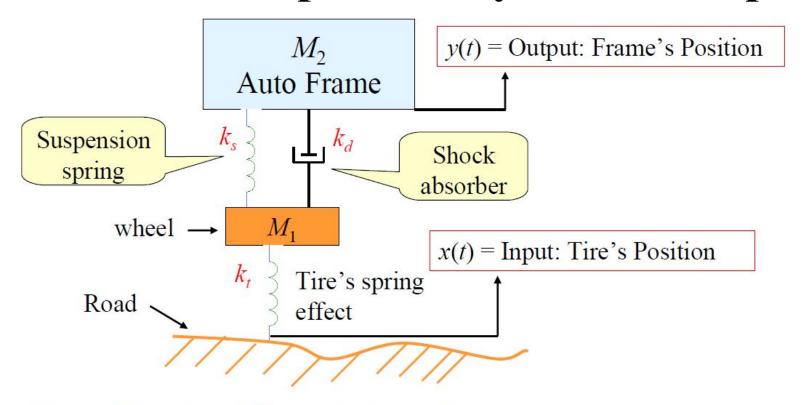

### Results in 4th order differential equation:

$$\frac{d^4 y(t)}{dt^4} + \frac{a_3 d^3 y(t)}{dt^3} + \frac{a_2 d^2 y(t)}{dt^2} + \frac{a_1 dy(t)}{dt} + a_0 y(t) = F[x(t)]$$

The  $a_i$  are functions of system's physical parameters:

$$M_1$$
,  $M_2$ ,  $k_s$ ,  $k_d$ ,  $k_t$ 

Some function of Input x(t)

# Again... to find the output for a given input requires solving the differential equation

Engineers could use this differential equation <u>model</u> to theoretically explore:

- 1. How the car will respond to some typical theoretical test inputs when different possible values of system physical parameters are used
- 2. Determine what the best set of system physical parameters are for a desired response
- 3. Then... maybe build a prototype and use it to fine tune the real-world effects that are not captured by this differential equation model

So... What we are seeing is that for an engineer to analyze or design a circuit (or a general physical system) there is almost always an underlying Differential Equation whose solution for a given input tells how the system output behaves

So... engineers need both a qualitative and quantitative understanding of Differential Equations.

The major goal of this course is to provide tools that help gain that qualitative and quantitative understanding!!!


Differential Equations like this are Linear and Time Invariant:


$$a_n \frac{d^n y(t)}{dt^n} + a_{n-1} \frac{d^{n-1} y(t)}{dt^{n-1}} + \dots + a_0 y(t) = b_m \frac{d^m f(t)}{dt^m} + \dots + b_1 \frac{df(t)}{dt} + b_0 f(t)$$

- -coefficients are constants  $\Rightarrow$  TI
- -No nonlinear terms  $\Rightarrow$  Linear

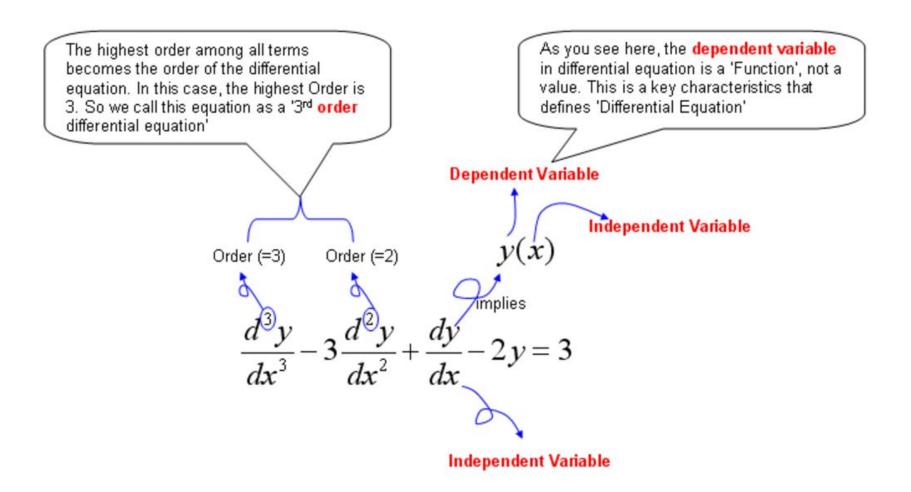Examples of Nonlinear Terms:


$$f^{n}(t)$$
,  $\left[\frac{d^{k}y(t)}{dt^{k}}\right]\left[\frac{d^{p}y(t)}{dt^{p}}\right]$ ,  $y^{n}(t)$ ,  $\left[\frac{d^{k}y(t)}{dt^{k}}\right]\left[\frac{d^{p}y(t)}{dt^{p}}\right]$ , etc.



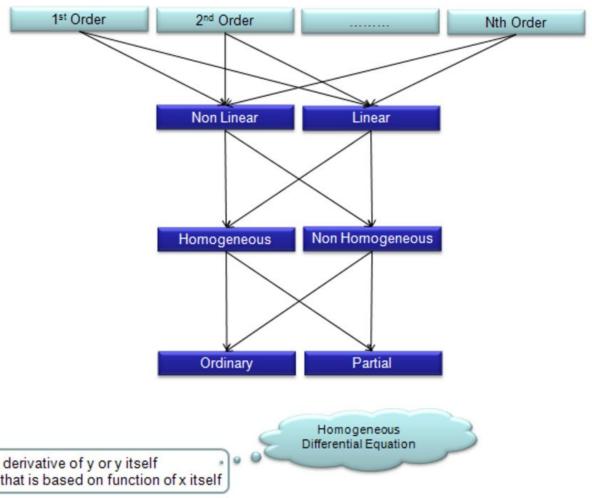

- All terms has the derivative of y or y itself
- There is no term that is based on function of x itself
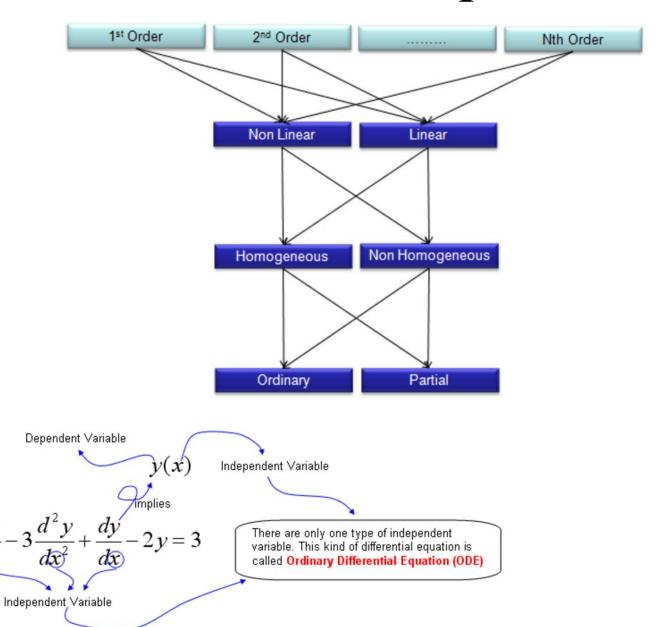
$$a_n y^{(n)} + a_{n-1} y^{(n-1)} + \dots + a_1 y' + a_0 y = 0$$



In the following we will BRIEFLY review the basics of solving Linear, Constant Coefficient Differential Equations under the Homogeneous Condition

"Homogeneous" means the "forcing function" is zero

That means we are finding the "zero-input response" that occurs due to the effect

of the initial coniditions.

We will assume:  $m \le n$ 

*m* is the highest-order derivative on the "input" side

*n* is the highest-order derivative on the "output" side

Use "operational notation": 
$$\frac{d^k y(t)}{dt^k} \equiv D^k y(t)$$

 $\Rightarrow$  Write D.E. like this:

$$\underbrace{\left(D^n + a_{n-1}D^{n-1} + \dots + a_1D + a_0\right)}_{\triangleq \mathcal{Q}(D)} y(t) = \underbrace{\left(b_m D^m + \dots + b_1D + b_0\right)}_{\triangleq P(D)} f(t)$$

Diff. Eq. 
$$\Rightarrow$$
  $Q(D)y(t) = P(D)f(t)$ 

<u>Due to linearity:</u> Total Response = Zero-Input Response + Zero-State Response

<u>Z-I Response</u>: found assuming the input f(t) = 0 but with given IC's

Z-S Response: found assuming IC's = 0 but with given f(t) applied

#### Finding the Zero-Input Response (Homogeneous Solution)

Assume f(t) = 0

$$\Rightarrow$$
 D.E.:  $Q(D)y_{zi}(t) = 0$ 

$$\Rightarrow D.E.. \mathcal{Q}(D)y_{zi}(t) = 0$$

$$\Rightarrow \left(D^n + a_{n-1}D^{n-1} + ... + a_1D + a_0\right)y_{zi}(t) = 0 \quad \forall t > 0$$



"linear combination" of  $y_{zi}(t)$  & its derivatives must be = 0

Consider  $y_0(t) = ce^{\lambda t}$ 

c and  $\lambda$  are possibly complex numbers

Can we find c and  $\lambda$  such that  $y_0(t)$  qualifies as a homogeneous solution?

Put  $y_0(t)$  into ( $\triangle$ ) and use result for the derivative of an exponential:  $\frac{d^n e^{\lambda t}}{dt^n} = \lambda^n e^{\lambda t}$ 

$$\frac{d^n e^{\lambda t}}{dt^n} = \lambda^n e^{\lambda t}$$

$$c(\underbrace{\lambda^{n} + a_{n-1}\lambda^{n-1} + \dots + a_{1}\lambda + a_{0}})e^{\lambda t} = 0$$

$$\text{must} = 0$$

 $c_1 e^{\lambda_1 t}$  is a solution  $c_2 e^{\lambda_2 t}$  is a solution :  $c_n e^{\lambda_n t}$  is a solution

Characteristic polynomial

 $Q(\lambda)$  has at most *n* unique roots

(can be complex)

$$\Rightarrow Q(\lambda) = (\lambda - \lambda_1)(\lambda - \lambda_2)...(\lambda - \lambda_n)$$


So...any linear combination is also a solution to  $(\triangle)$ 

Z-I Solution: 
$$y_{zi}(t) = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t} + ... + c_n e^{\lambda_n t}$$

Then, choose  $c_1, c_2, ..., c_n$  to satisfy the given IC's


$$\{e^{\lambda_i t}\}_{i=1}^n$$
 Set of characteristic modes

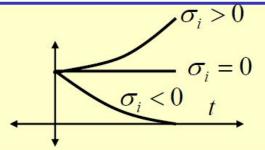
Real Root: 
$$\lambda_i = \sigma_i + j0 \implies e^{\sigma_i t}$$
real real



Complex Root:  $\lambda_i = \sigma_i + j\omega_i$ 

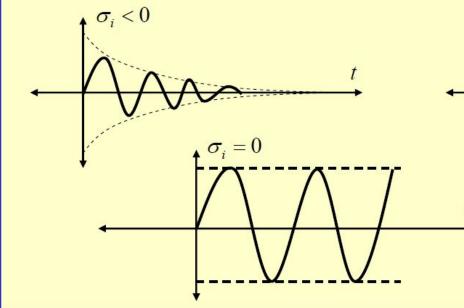Mode:  $e^{\lambda_i t} = e^{\sigma_i t} + e^{j\omega_i t}$ 



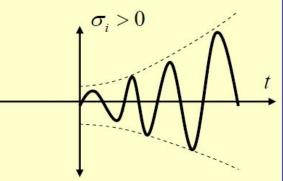

To get only real-valued solutions requires the system coefficients to be real-valued.

 $\Rightarrow$  Complex roots of C.E. will appear in conjugate pairs:

$$\lambda_{i} = \sigma + j\omega$$

$$\lambda_{k} = \sigma - j\omega$$
Conjugate pair

$$c_{i}e^{\lambda_{i}t} + c_{k}e^{\lambda_{k}t} = c_{i}e^{\sigma t}e^{j\omega t} + c_{k}e^{\sigma t}e^{j\omega t}$$

$$\frac{C}{2}e^{j\theta} \qquad \frac{C}{2}e^{-j\theta}$$
For some real  $C$ 

Use Euler!  $Ce^{\sigma t}\cos(\omega t + \theta)$  t > 0

### Repeated Roots

Say there are *r* repeated roots

$$Q(\lambda) = (\lambda - \lambda_1)^r (\lambda - \lambda_2)(\lambda - \lambda_3)...(\lambda - \lambda_p) \qquad p = n - r$$

We "can verify" that:  $e^{\lambda_i t}$ ,  $te^{\lambda_1 t}$ ,  $t^2 e^{\lambda_1 t}$ , ...,  $t^{r-1} e^{\lambda_1 t}$  satisfy ( $\triangle$ )

#### ZI Solution:

$$y_{zi}(t) = (c_{11} + c_{12}t + \dots + c_{1r}t^{r-1})e^{\lambda_i t} + \text{other modes}:$$
effect of *r*-repeated roots

### **Differential Equation Examples**

Find the zero-input response (i.e., homogeneous solution) for these three Differential Equations.

### Example (a)

$$\frac{d^{2}y(t)}{dt^{2}} + 3\frac{dy(t)}{dt} + 2y(t) = \frac{df(t)}{dt}$$

$$\frac{\mathbf{w}/\mathbf{I.C.'s}}{dt}$$

$$y(0)=0, y'(0)=-5$$

$$D^{2}y(t) + 3Dy(t) + 2y(t) = Df(t)$$

The zero-input form is:

$$\frac{d^2y(t)}{dt^2} + 3\frac{dy(t)}{dt} + 2y(t) = 0$$
$$D^2y(t) + 3Dy(t) + 2y(t) = 0$$

The Characteristic Equation is:

$$\lambda^2 + 3\lambda + 2 = 0 \implies (\lambda + 1)(\lambda + 2) = 0$$

### The Characteristic Equation is:

$$\lambda^2 + 3\lambda + 2 = 0 \implies (\lambda + 1)(\lambda + 2) = 0$$

The Characteristic Roots are:

$$\lambda_1 = -1$$
 &  $\lambda_2 = -2$ 

The Characteristic "Modes" are:

$$e^{\lambda_1 t} = e^{-t}$$
 &  $e^{\lambda_2 t} = e^{-2t}$ 

The zero-input solution is:

$$y_{zi}(t) = C_1 e^{-t} + C_2 e^{-2t}$$

The <u>System</u> forces this form through its Char. Eq.

The <u>IC's</u> determine the specific values of the  $C_i$ 's

The zero-input solution is:

$$y_{zi}(t) = C_1 e^{-t} + C_2 e^{-2t}$$

and it must satisfy the ICs so:

$$0 = y_{zi}(0) = C_1 e^{-0} + C_2 e^{-0} \implies C_1 + C_2 = 0$$

The derivative of the z-s soln. must also satisfy the ICs so:


$$-5 = y'_{zi}(0) = -C_1 e^{-0} - 2C_2 e^{-0} \implies C_1 + 2C_2 = 5$$

Two Equations in Two Unknowns leads to:

$$C_1 = -5$$
 &  $C_2 = 5$ 

The "particular" zero-input solution is:
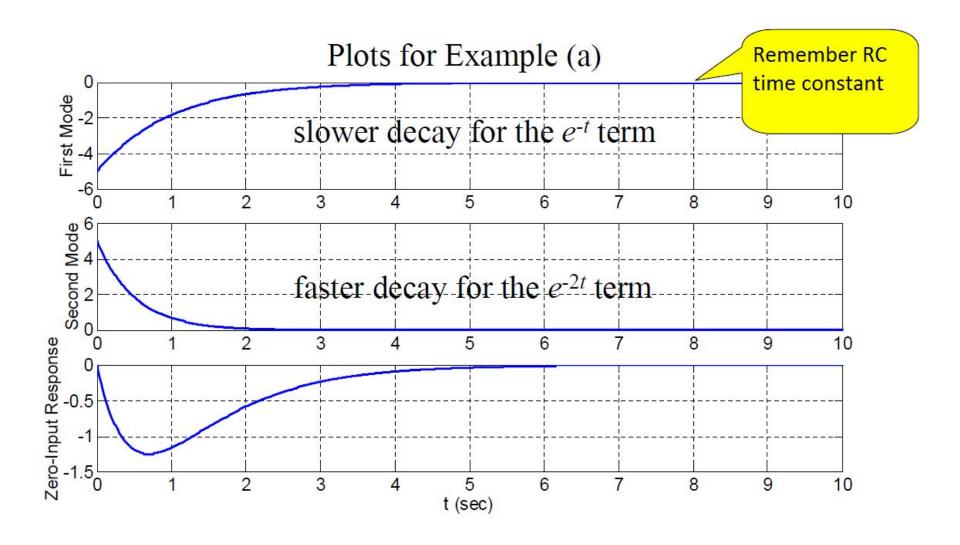
$$y_{zi}(t) = \underline{-5e^{-t}} + \underline{5e^{-2t}}$$
first mode second mode



Because the characteristic roots are <u>real and negative</u>... the modes and the Z-I response all <u>decay to zero w/o oscillations</u>

### Example (b):

$$\frac{d^2y(t)}{dt^2} + 6\frac{dy(t)}{dt} + 9y(t) = 3\frac{df(t)}{dt} + 5f(t)$$

$$\frac{\mathbf{W}/\mathbf{I.C.'s}}{dt^2}$$

$$y(0) = 3, y'(0) = -7$$

$$D^2y(t) + 6Dy(t) + 9y(t) = 3Df(t) + 5f(t)$$

The zero-input form is:

$$\frac{d^2y(t)}{dt^2} + 6\frac{dy(t)}{dt} + 9y(t) = 0$$
$$D^2v(t) + 6Dv(t) + 9v(t) = 0$$

The Characteristic Equation is:

$$\lambda^2 + 6\lambda + 9 = 0 \implies (\lambda + 3)^2 = 0$$

### The Characteristic Equation is:

$$\lambda^2 + 6\lambda + 9 = 0 \implies (\lambda + 3)^2 = 0$$

The Characteristic Roots are:

$$\lambda_1 = -3$$
 &  $\lambda_2 = -3$ 

Real, repeated roots

The Characteristic "Modes" are:

$$e^{\lambda_1 t} = e^{-3t}$$
 &  $te^{\lambda_2 t} = te^{-3t}$ 

Using the "rule" to handle repeated roots

The zero-input solution is:

$$y_{zi}(t) = C_1 e^{-3t} + C_2 t e^{-3t}$$


The <u>System</u> forces this form through its Char. Eq.

The <u>IC's</u> determine the specific values of the  $C_i$ 's

Following the same procedure (do it for yourself!!) you get...

The "particular" zero-input solution is:
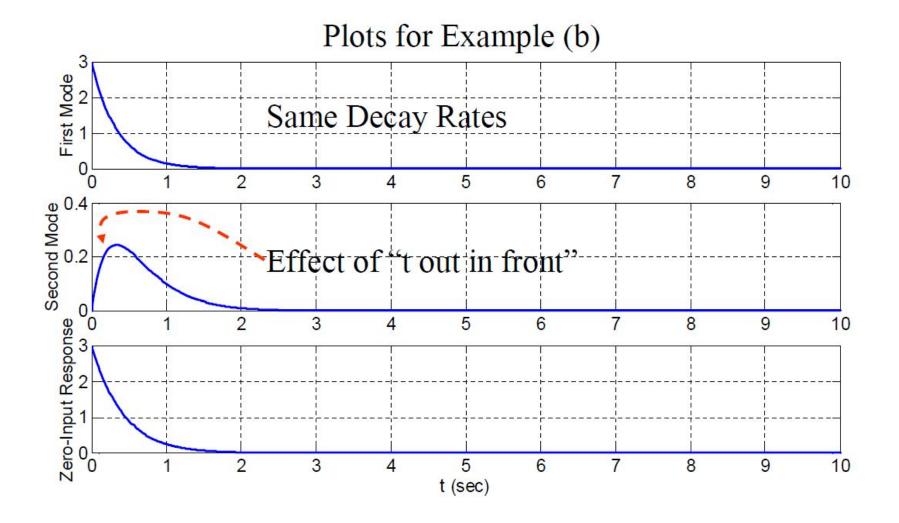
$$y_{zi}(t) = \underbrace{3e^{-3t}}_{\text{first mode}} + \underbrace{2te^{-3t}}_{\text{second mode}} = (3+2t)e^{-3t}$$



Because the characteristic roots are <u>real and negative</u>... the modes and the Z-I response all <u>decay to zero w/o oscillations</u>

### Example (c):

$$\frac{d^2y(t)}{dt^2} + 4\frac{dy(t)}{dt} + 40y(t) = \frac{df(t)}{dt} + 2f(t)$$

$$\frac{\mathbf{w}/\mathbf{I.C.'s}}{dt}$$

$$y(0) = 2, y'(0) = 16.78$$

$$D^2y(t) + 4Dy(t) + 40y(t) = Df(t) + 2f(t)$$

The zero-input form is:

$$\frac{d^2y(t)}{dt^2} + 4\frac{dy(t)}{dt} + 40y(t) = 0$$
$$D^2v(t) + 4Dv(t) + 40v(t) = 0$$

The Characteristic Equation is:

$$\lambda^2 + 4\lambda + 40 = 0 \implies (\lambda + 2 - j6)(\lambda + 2 + j6) = 0$$

### The Characteristic Equation is:

$$\lambda^2 + 4\lambda + 40 = 0 \implies (\lambda + 2 - j6)(\lambda + 2 + j6) = 0$$

The Characteristic Roots are:

$$\lambda_1 = -2 + j6$$
 &  $\lambda_2 = -2 - j6$ 

complex conjugate roots

### The Characteristic "Modes" are:

$$e^{\lambda_1 t} = e^{-2t} e^{+j6t}$$
 &  $e^{\lambda_2 t} = e^{-2t} e^{-j6t}$ 

The zero-input solution is:


$$y_{zi}(t) = C_1 e^{-2t} e^{+j6t} + C_2 e^{-2t} e^{-j6t}$$


The <u>System</u> forces this form through its Char. Eq.

The <u>IC's</u> determine the specific values of the  $C_i$ 's

Following the same procedure with some manipulation of complex exponentials into a cosine...

The "particular" zero-input solution is:

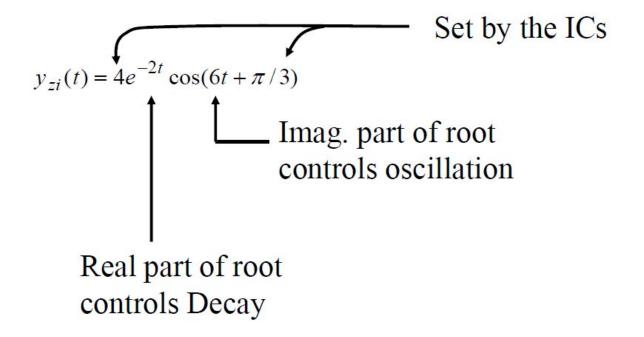

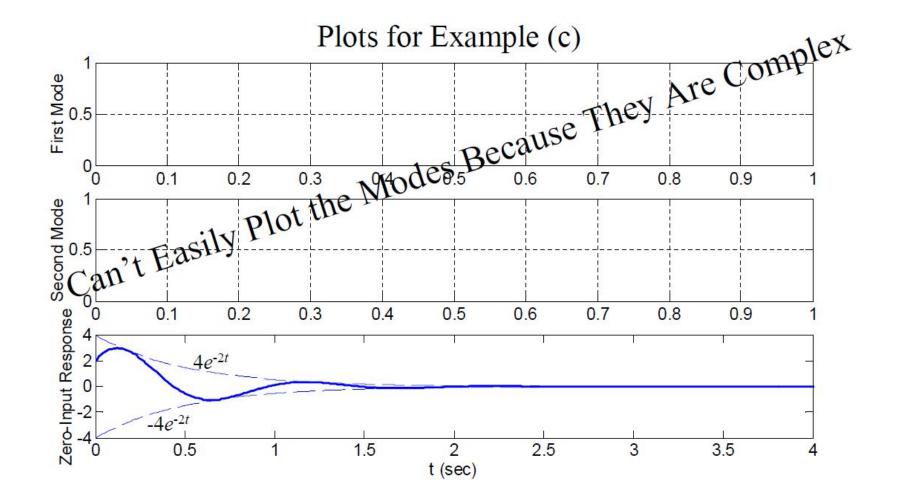

Because the characteristic roots are <u>complex</u>... have oscillations! Because real part of root is negative... <u>decays to zero</u>!!!

https://www.youtube.com/watch?v=XggxeuFDaDU

# Tacoma Bridge Collapse: The Wobbliest Bridge in the World? (1940)

### Big Picture...

The <u>structure</u> of the D.E. determines the char. roots, which determine the "character" of the response:

- Decaying vs. Exploding (controlled by real part of root)
- Oscillating or Not (controlled by imag part of root)

The D.E. structure is determined by the physical system's structure and component values.